

The Superior University, Lahore

(A GOVERNMENT CHARTERED UNIVERSITY)

Serial No:

135776

Student's Name: Ayesha Usrooj
Program: BSCS (Bachelors in Computer Science)
Section: 1C (BSCS-1C)

Roll No: 107 (SU92-bsscm-f22-107)

Subject: Applied Physics

Date: 19th Jan, 2023

Semester: 1st (First)

Invigilator's Signature: _____

Total Number of Continuation Sheet: _____

Questions	1	2	3	4	5	6	7	8	9	10
Marks Obtained										

Examiner's Signature: _____

Please start to write from here

SUBJECTIVE TYPE


Question no :- 1

(A)

4/8/


Practical Diode:-

Forward Biasing:-

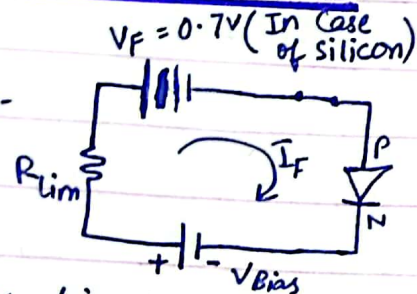

In practical Model; In the case of forward biasing we always use switch on circuit. R_{Lim} shows limited resistance. V_F shows forward Voltage.

Reverse Biasing:-

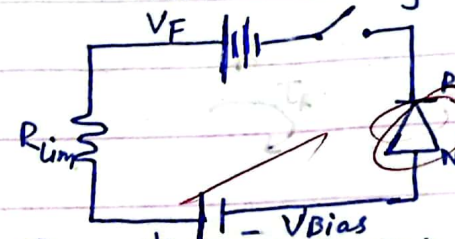

In reverse (case) biasing, we always use switch off circuit. No current is produced in reverse. Current is not produce

	V_F	r'_d	r'_f
Practical Model	✓	✗	✗
Complete Model	✓	✓	✓

Formula :-

$$I_F = \frac{V_{Bias} - V_F(0.7)}{R_{lim}}$$


$V_{Bias} \Rightarrow$ Biased Voltage

$V_F \Rightarrow$ Forward Voltage


$R_{lim} \Rightarrow$ limited resistance.

$\therefore \Rightarrow V_F = 0.7V$ in case of Silicon & In case of Germanium it is $0.3V$

Complete Model

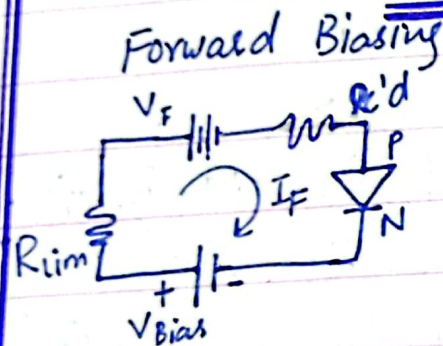

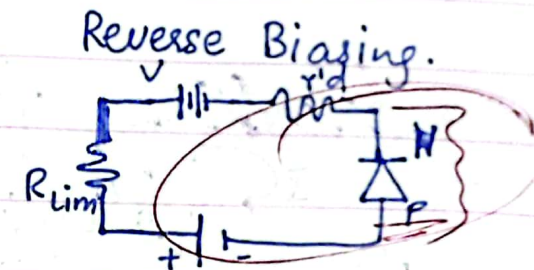In forward biasing case of complete circuit a resistor is added. r_d shows dynamic resistance.



In reverse biasing case of complete circuit. A resistor is added that shows dynamic resistance. Battery shows Voltage.

Formula:-

$$I_F = \frac{V_{bias} - V_F (0.7V \text{ in silicon case})}{R_{lim} - R_d}$$

$R_d \Rightarrow$ Dynamic Resistance


$R_{lim} \Rightarrow$ Limited Resistance

(B)


Working of Diode:-

A diode is formed in PN-Junction. In PN-Junction, a barrier is formed/produced by the flow of free electron. Free electron formed a barrier between the P type & N type which is known as potential barrier (Diode).

Diode is usually represented as:-

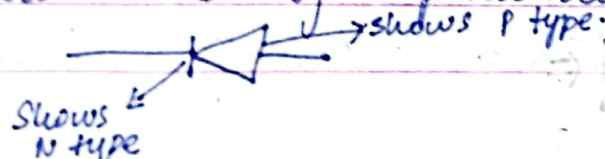


(Page Turn Over)

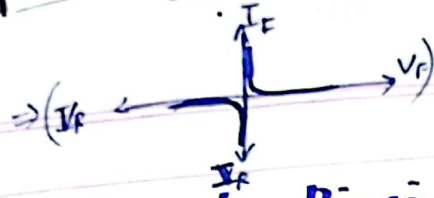


Forward Biasing:-

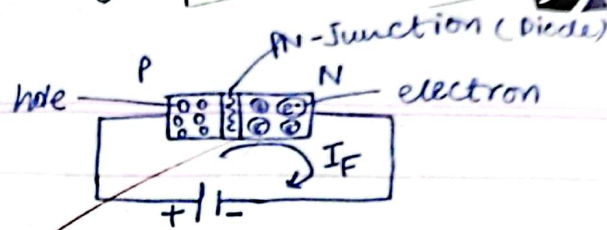In forward Biasing, "P Type" is connected with the "positive terminal" of the battery and "N type" is connected with the "negative terminal" of the battery. "P type" contains "Majority of holes" & "minority of electrons". Some of the free electrons flow & produced "Forward Current" (represented by I_F). In forward biasing, we use switch on circuit. $\Rightarrow V_F > V_{Bias}$



Reverse Biasing:-

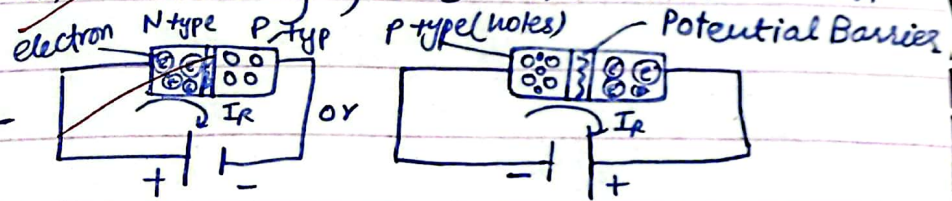In reverse biasing, "P type semi conductor" is connected with the "negative terminal" of battery & "N type semi conductor" is connected with the "positive terminal" of the battery. Potential Barrier separated P type from N type. A little bit Reverse Current is produced in it. Current Increases Abruptly at Breakdown point.




(C)

N type Semiconductors:-

(In N type semi-conductors) a pentavalent impurity is added in pure semi conductor to make it Extrinsic Semi-conductor. A tri-valent impurity is added in the pure semi-conductor.

N-type semi-conductors Contain:-



Majority of Electrons
Minority of holes

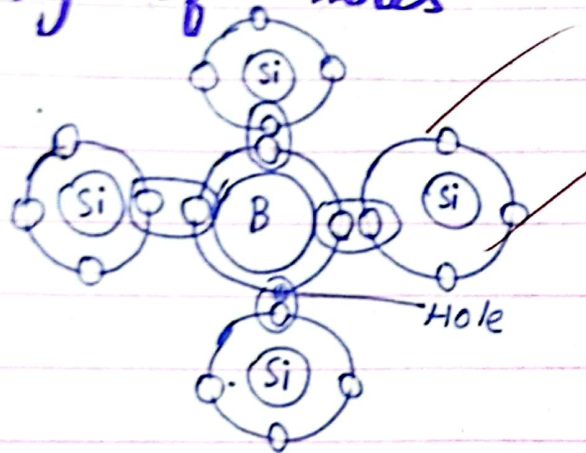

P-Type :-

In P type Semiconductor a pentavalent impurity is added in the pure form of Semiconductor. P type contains holes (mostly). Holes are positively charged carriers.

Majority of Holes
Minority of Electrons

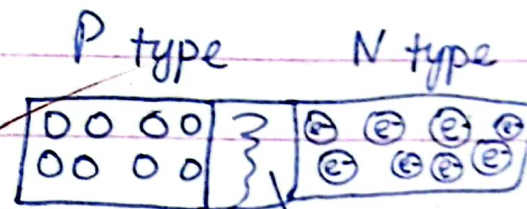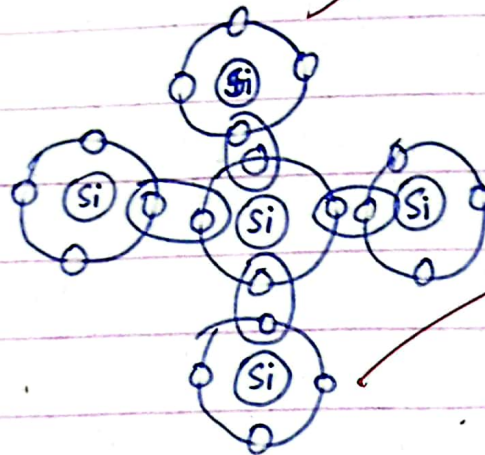

Potential
Barrier

Question no:- 2

(B)

Given:- $R_1 = 220 \Omega$, $R_2 = 470 \Omega$, $R_3 = 470 \Omega$
 $I_s = 4 \text{ mA}$

To find:- $I_1 = ?$, $I_2 = ?$, $I_3 = ?$

Sol:- using CDR

$$I_x = \left(\frac{R_t}{R_x} \right) I_s$$

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

\therefore Parallel circuit.

$$\frac{1}{R_t} = \frac{1}{220} + \frac{1}{470} + \frac{1}{470} = 8.8 \times 10^{-3} \Omega^{-1}$$

$$R_t = \frac{1}{8.8 \times 10^{-3}} \approx 113.63 \Omega$$

$$R_t = 113.63 \Omega$$

$$I_1 = \left(\frac{113.63}{220} \right) (4 \times 10^{-3}) = 2.066 \text{ mA} = 2.066 \times 10^{-3} \text{ A}$$

$$I_2 = \left(\frac{113.63}{470} \right) (4 \times 10^{-3}) = 9.67 \times 10^{-4} \text{ A} = 0.967 \times 10^{-3} \text{ A}$$

$$\Rightarrow I_2 = 0.967 \text{ mA} \approx 0.97 \text{ mA}$$

$$I_3 = \left(\frac{113.63}{470} \right) (4 \times 10^{-3}) = 0.967 \times 10^{-3} \text{ A}$$

$$\Rightarrow I_3 = 0.97 \text{ mA}$$

So,

$$I_1 = 2.06 \text{ mA}$$

$$I_2 = 0.97 \text{ mA}$$

$$I_3 = 0.97 \text{ mA}$$

(A)

Given:-

$$R_1 = 560 \Omega, R_2 = 330 \Omega, R_3 = 330 \Omega, R_4 = 560 \Omega$$

$$V_s = 48V$$

∴ In parallel circuit voltage is same

To find:- $I_1 = ?$, $I_2 = ?$, $I_3 = ?$, $I_4 = ?$

Solution:-

$$V = IR$$

$$\frac{V}{R_1} = I_1$$

$$I_1 = \frac{48}{560}$$

$$\Rightarrow = 0.085714$$

$$I_1 \approx 0.09 A$$

$$I_2 = \frac{V}{R_2}$$

$$I_2 = \frac{48}{330}$$

$$= 0.1454545455$$

$$I_2 \approx 0.15 A$$

$$I_3 = \frac{V}{R_3} = \frac{48}{330} \Rightarrow I_3 = 0.15 A$$

$$I_4 = \frac{V}{R_4} = \frac{48}{560} \Rightarrow I_4 = 0.09 A$$

(C)

Given:- $P_2 = 0.75 W$
 $V_s = ?$

$$I_1 = ?$$

$$I_2 = ?$$

$$P_T = 2W$$

$$R_1 = ?$$

$$R_2 = ?$$

$$I_T = 200 mA$$

Sol:- $P = VI$

Circuit is a parallel circuit \Rightarrow Voltage is same in para

$$P_2 = VI$$

$$\frac{P_2}{I} = V$$

$$\Rightarrow \frac{2}{200 \times 10^{-3}} = V_s \Rightarrow V_s = 10 V$$

$$P_T = V_s I_T$$

$$\frac{P_T}{I_T} = V_s$$

$$V_s = 10 V$$

Voltage is 10 V.

$$P_2 = VI_2$$

$$\frac{P_2}{I_2} = V \Rightarrow \frac{P_2}{V} = I_2$$

$$I_2 = \frac{0.75}{10} = 0.075 \text{ A}$$

$$V = I_2 R_2 \Rightarrow \frac{V}{I_2} = R_2$$

$$R_2 = \frac{10}{0.075} = 133.3 \, \Omega$$

$$P_T = P_1 + P_2 \Rightarrow P_T - P_2 = P_1 \Rightarrow P_1 = 1.25 \text{ W}$$

$$P_1 = VI_1$$

$$I_1 = \frac{P_1}{V} = \frac{1.25}{10} \Rightarrow I_1 = 0.125 \text{ A}$$

$$V = I_1 R_1 \Rightarrow \frac{V}{I_1} = R_1 \Rightarrow R_1 = \frac{10}{0.125} = 80 \, \Omega$$